

Circuit Demonstration Page

Student names: Forrest Knee _____

Instructor Initials

Pushbutton "Or Gate"

Ked

Transistor Not gate

Ked

Transistor Nor gate

Ked

Transistor unknown gate

Ked

Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.

Inverter:

