

# ELC 2137 Lab 5: Intro to Verilog

Forrest Knee

March 3, 2021

## Summary

This lab involved creating a half adder, full adder, and 2-bit adder/subtractor and simulating them in verilog.

## Q&A

4. Do the simulations match the expected output values?

Yes, my simulations do perform as expected.

5. What is one thing that you still don't understand about verilog?

There are many many options that we were told to skip through and select certain settings when creating our project and file. I did not understand many of those choices.

## Results

Name	Value	0.000 ns	5.000 ns	10.000 ns	15.000 ns	20.000 ns	25.000 ns	30.000 ns	35.000 ns
a1	1								
b1	1								
carry1	1								
sum1	0								

Figure 1: Half Adder

 


Figure 2: Full Adder


 


Figure 3: 2 Bit Adder Subtractor

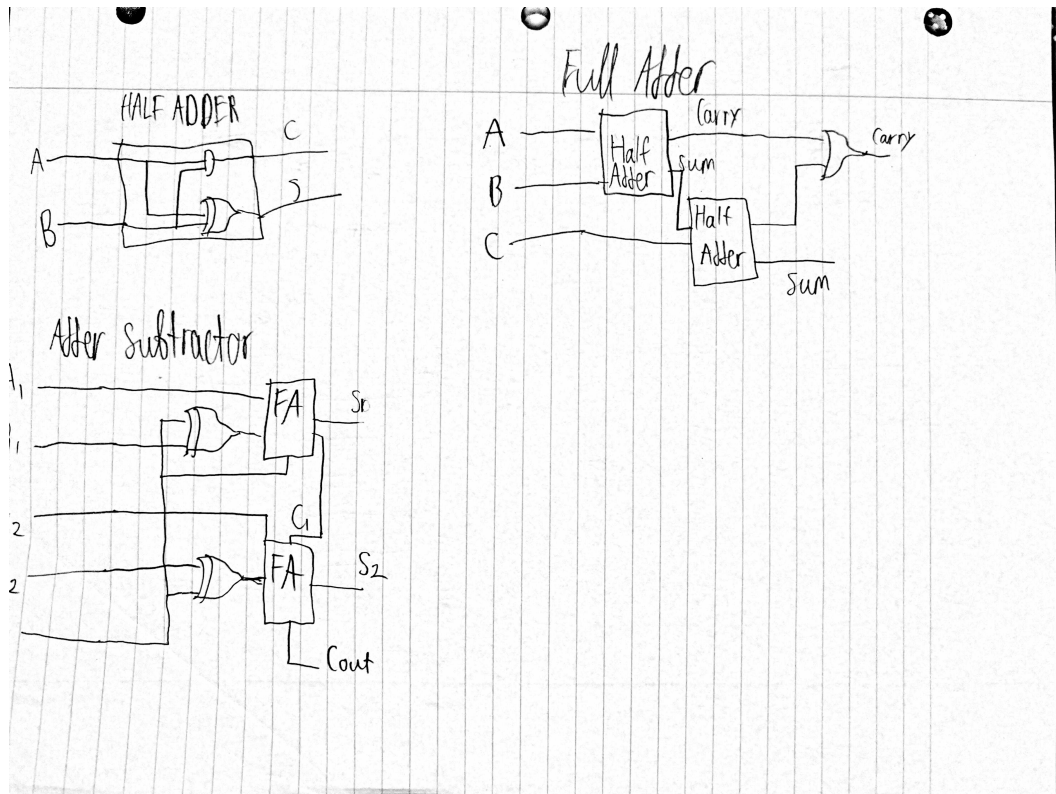

## Code

Listing 1: Half Adder

```
'timescale 1ns / 1ps
//Forrest Knee

module halfadder(
    input a,b,
    output c,s);

    assign c=(a&b);
    assign s=(a^b);

endmodule
```

Listing 2: Half Adder Test

```
'timescale 1ns / 1ps
//Forrest Knee

module halfadder_SIM();

    reg a1,b1;
    wire carry1,sum1;

    halfadder ha1(
        .a(a1), .b(b1), .c(carry1), .s(sum1));

    initial begin

        //case 1

        a1=0; b1=0;
        #10;

        //case 2

        a1=0; b1=1;
        #10

        //case 3

        a1=1; b1=0;
        #10

        //case 4

        a1=1; b1=1;
        #10
```

```
    $finish;
    end

endmodule
```

---

### Listing 3: Full Adder

---

```
'timescale 1ns / 1ps

// Forrest Knee

module fulladder(

    input a1,b1,cin,
    output s,c
);

    wire s1,c1,c2;

    halfadder ha1(
        .a(a1), .b(b1), .c(c1), .s(s1));

    halfadder ha2(
        .a(cin), .b(s1), .c(c2), .s(s));

    assign c=(c1 | c2);

endmodule
```

---

### Listing 4: Full Adder Test

---

```
'timescale 1ns / 1ps

//Forrest Knee

module fulladder_SIM();

    reg a1,b1,cin;
    wire c,s;

    fulladder fa1(

        .a1(a1), .b1(b1), .cin(cin), .c(c), .s(s));

    initial begin

        //case 1
        a1 = 0;
        b1 = 0;
        cin = 0;
        #10
```

```

        //case 2
a1 = 0;
b1 = 1;
cin = 0;
#10

        //case 3
a1 = 1;
b1 = 0;
cin = 0;
#10

        //case 4
a1 = 1;
b1 = 1;
cin = 0;
#10

        //case 5
a1 = 0;
b1 = 0;
cin = 1;
#10

        //case 6
a1 = 0;
b1 = 1;
cin = 1;
#10

        //case 7
a1 = 1;
b1 = 0;
cin = 1;
#10

        //case 8
a1 = 1;
b1 = 1;
cin = 1;
#10
$finish;
end

endmodule

```

---

Listing 5: 2 Bit Adder Subtractor

---

```

`timescale 1ns / 1ps

//Forrest Knee

```

```

module addersubtractor(
    input a1,b1,a2,b2,k,
    output s1,s2,c2);

    wire cb1, cb2, c1;

    assign cb1=(b1^k);
    assign cb2=(b2^k);

    fulladder fa1(
        .a1(a1), .b1(cb1), .cin(k), .c(c1), .s(s1));

    fulladder fa2(
        .a1(a2), .b1(cb2), .cin(k), .c(c2), .s(s2));

endmodule

```

---

Listing 6: 2 Bit Adder Subtractor Test

---

```

`timescale 1ns / 1ps
//Forrest Knee

module addsub_SIM();

    reg a1,b1,a2,b2,k;
    wire s1,s2,c2;

    addersubtractor as1(

        .a1(a1), .b1(b1), .a2(a2), .b2(b2), .k(k), .s1(s1), .s2(s2), .c2(c2)
    );

    initial begin

        // Case 1
        a1= 0;
        b1= 1;
        a2= 0;
        b2= 0;
        k= 0;
        #10;
        // Case 2
        a1= 0;
        b1= 0;
        a2= 0;
        b2= 1;
        k= 0;
        #10
    end

```

```

// Case 3
a1= 0;
b1= 1;
a2= 0;
b2= 1;
k= 0;
#10
// Case 4
a1= 1;
b1= 1;
a2= 0;
b2= 0;
k= 0;
#10
// Case 5
a1= 0;
b1= 1;
a2= 1;
b2= 0;
k= 0;
#10
// Case 6
a1= 0;
b1= 0;
a2= 1;
b2= 0;
k= 0;
#10
// Case 7
a1= 0;
b1= 1;
a2= 0;
b2= 0;
k= 1;
#10
// Case 8
a1= 0;
b1= 0;
a2= 0;
b2= 1;
k= 1;
#10
// Case 9
a1= 0;
b1= 1;
a2= 0;
b2= 1;
k= 1;
#10
// Case 10
a1= 1;
b1= 1;
a2= 0;
b2= 0;

```

```
k= 1;
#10
// Case 11
a1= 0;
b1= 1;
a2= 1;
b2= 0;
k= 1;
#10
// Case 12
a1= 0;
b1= 0;
a2= 1;
b2= 0;
k= 1;
#10

$finish;

end

endmodule
```

---