

ELC 2137 Lab 2: Transistors

Forrest Knee

February 3, 2021

Summary

This lab's focus was making different physical logic gates using transistors. The gates built were an OR, AND, NOT, and NOR gate.

Q&A

1. What is the Logic/truth table for the final gate?

A	B	OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

2. What logic operation does it implement?

AND

Results

ELC 2137

Lab 2. Transistor Logic Gates

Circuit Demonstration Page

Student names: Forrest Knee _____

Instructor Initials

Pushbutton "Or Gate"

Keg

Transistor Not gate

Keg

Transistor Nor gate

Keg


Transistor unknown gate

Keg


Diagrams

On each of the circuits below, draw the current paths and note whether each switch, transistor, and LED is ON or OFF.


Inverter:

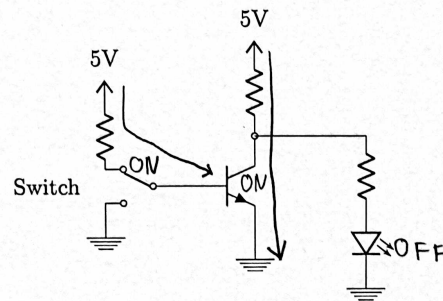

NOR:

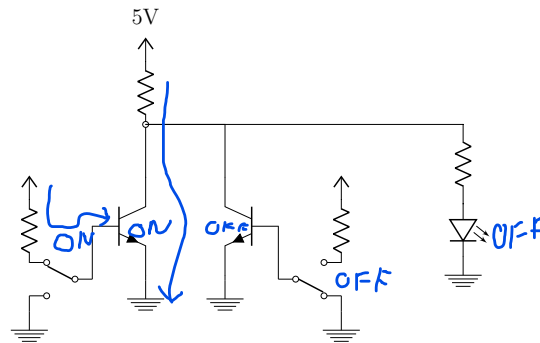

Final gate:

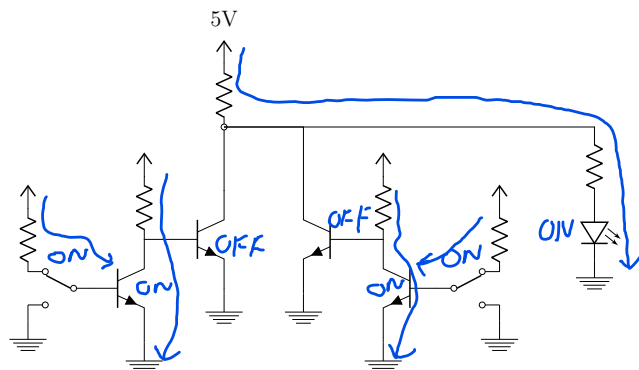**Code**

none