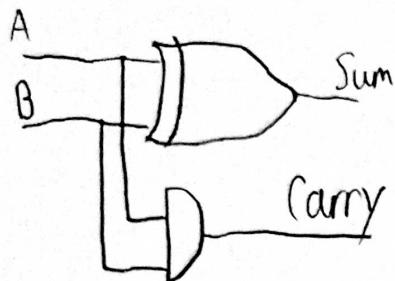
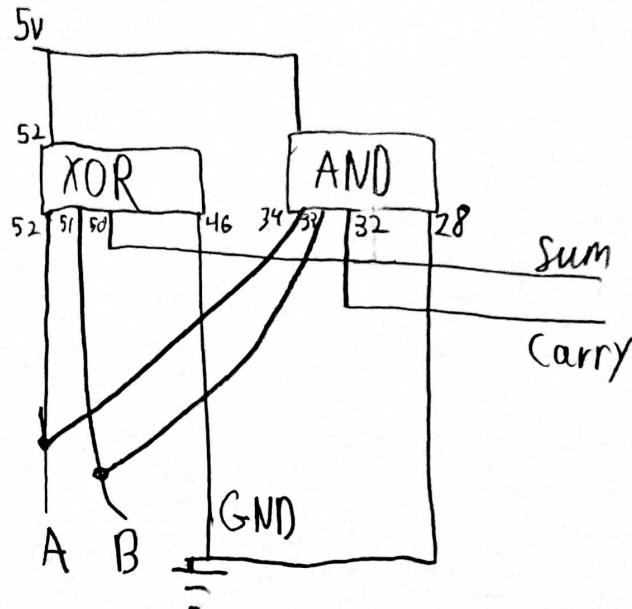
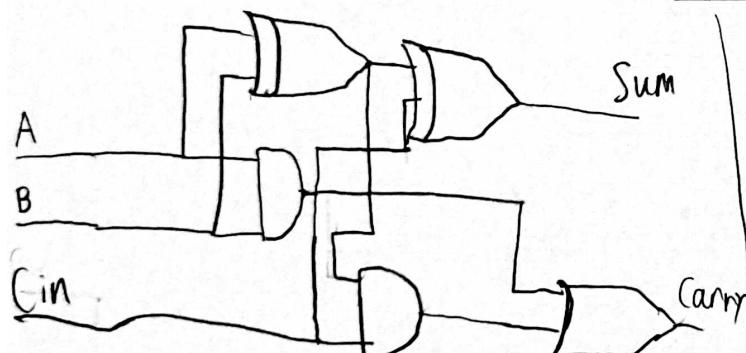
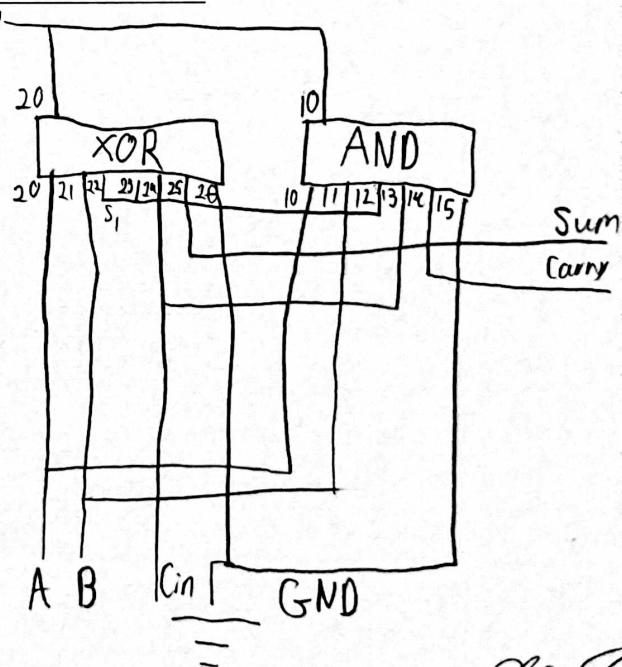


Circuit Demonstration Page

Half adder schematicHalf adder wiring diagramHalf adder: KelFull adder schematicFull adder wiring diagramFull adder: Kel2-bit adder: Kel