

Circuit Demonstration Page

Student names:

Forrest Knee

Instructor Signatures

Separate Full Adders



Two-Bit Adder



Adder/Subtractor



Inputs		Expected Results			Actual Results
A	B	B 2's comp	Sub	Dec	Sub
000	001	111	111	-1	111
000	010	110	110	-2	110
000	011	101	101	-3	101
001	001	111	000	0	000
010	001	111	001	1	001
010	000	000	010	2	010