

# ELC 2137 Lab 4: Subtractor

Forrest Knee

February 24, 2021

## Summary

This lab involved adding onto our adder circuit to make a subtractor. A key component was converting the input into a 2's compliment.

## Q&A

1. Two full adders were used at recommendation of the book.
2. There are 32 required combinations.
3. The table covers no duplicate results that require the same circuit elements.
4. I obtained no discrepancies in my data compared to expectations.

## Deliverables


ELC 2137 Lab 4. Subtractor


**Circuit Demonstration Page**


Student names: Forrest Knee

---

**Instructor Signatures**

Separate Full Adders 

Two-Bit Adder 

Adder/Subtractor 

Inputs		Expected Results			Actual Results
A	B	B 2's comp	Sub	Dec	Sub
000	001	111	111	-1	111
000	010	110	110	-2	110
000	011	101	101	-3	101
001	001	111	000	0	000
010	001	111	001	1	001
010	000	000	010	2	010

4

Figure 1: Demonstration Page

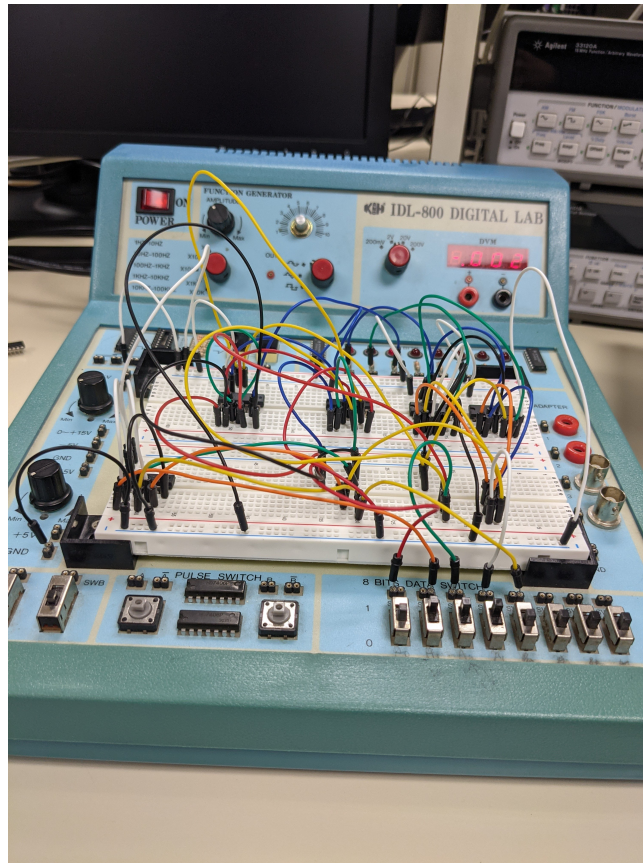


Figure 2: Subtractor

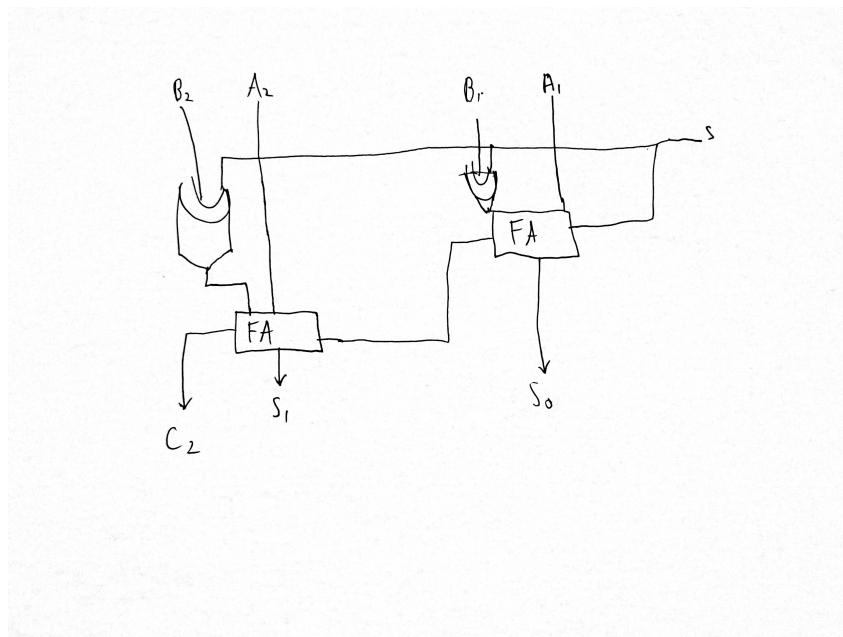


Figure 3: Schematic