

ELC 2137 Lab 3: Adders

Forrest Knee

February 24, 2021

Summary

This lab involved the use of AND and XOR IC's to make adders. We were tasked with building half, full, and eventually a 2 bit adder.

Q&A

Answer questions posed in the lab assignment here.

Results

In this section, put your simulation waveforms, results tables, pictures of hardware, and any other required items.

Code

Include all of the code you wrote or modified here.